
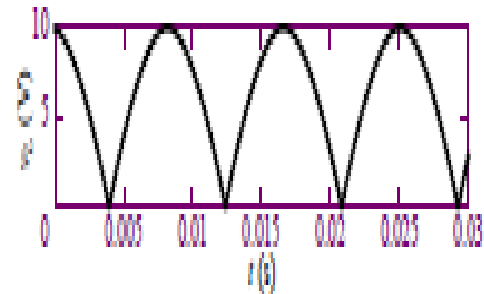
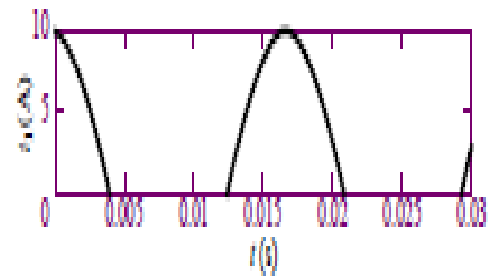
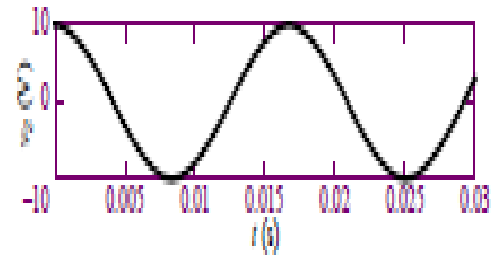


Full -wave Rectifier

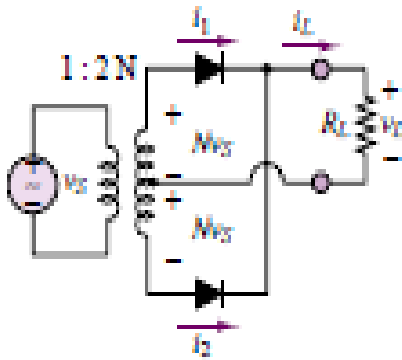The full wave rectifier circuit using two diodes and a center tapped transformer is shown in fig.3. The centers tap. is usually taken as the ground or zero voltage reference point.



(a) Working:

When input ac supply is switched on, the ends of the transformer secondary become +Ve and negative alternately. During the positive half cycle of the ac input. Hence, being forward biased diode D_1 conducts (but not D_2 which is reverse biased). As a result, positive half cycle of the voltage appears across R_L . In the negative half cycle D_2 conducts (but not D_1). So we find that current keeps on following through R_L in the same direction in both half cycles of the ac input. Also, the frequency of the rectified output voltage is twice the supply frequency.

(b) Average values:

$$\begin{aligned} \text{(i)} \quad V_{dc} &= \frac{2V_m}{\pi} \\ &= 0.636 V_m \text{ twice the half wave rectifier value} \\ &= \frac{2\sqrt{2}V}{\pi} = 0.9 V \end{aligned}$$

Where V_m is the maximum voltage across each half of the secondary winding.

$$V = \frac{V_m}{\sqrt{2}}$$

=rms voltage across each half of the secondary winding.

$$\begin{aligned} \text{(ii)} \quad I_{dc} &= \frac{2I_m}{\pi} = \frac{2}{\pi} \frac{V_m}{R_L} \\ &= 0.636 I_m \end{aligned}$$

$$= \frac{V_{dc}}{R} = \frac{2 \cdot \sqrt{2}}{\pi} \cdot \frac{V}{R_L}$$

$$= 0.9 \frac{V}{R_L}$$


$$(iii) \quad I_{rms} = 0.707 I_m$$

$$(iv) \quad \text{form factor, } F = \frac{I_{rms}}{I_{av}} = \frac{I_{rms}}{I_{dc}}$$

$$= \frac{0.707 I_m}{0.636 I_m} = 1.11$$

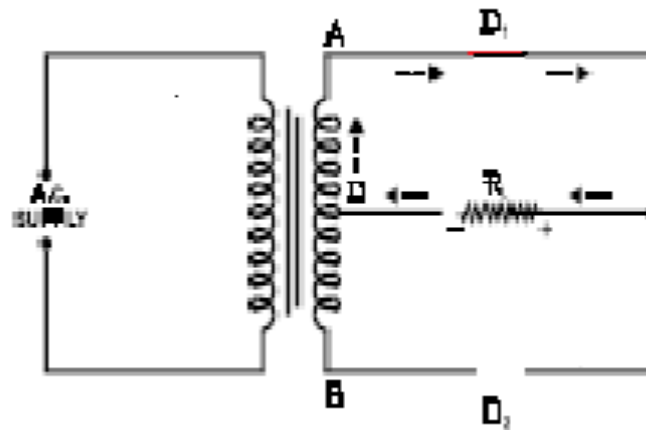(c) PIV:

In this case, PIV rating of each diode is $2 V_m$. consider the positive half cycle of the input ac supply when D_1 acts as short and D_2 acts as open since it is reverse biased. A voltage V_m develops across R_L . As seen from fig. below, voltage across D_2 is equal to the sum of voltages across the lower half GN of the transformer secondary and the load resistor. Hence PIV of $D_2 = 2 V_m$.



(d) Ripple factor (γ):

For full wave rectifier circuit $\gamma = \frac{V_r(rms)}{V_{dc}} = \frac{0.305 V_m}{0.636 V_m} = 0.482$

Is much less than that of half wave rectifier. The relation between V_m and V_{dc} is the same as HW rectifier.

(e) Efficiency:

$$\eta = \frac{P_{out}}{P_{in}}$$

$$= \frac{I_{dc}^2 * R_L}{I_{rms}^2 (r_d + R_L)}$$

Substituting and simplifying, we get

$$\eta = \frac{81.2\%}{1 + \frac{r_d}{R_L}} = 81.2\% \text{ if } r_d = 0$$

It is twice the value for half wave rectifier.


Full-Wave Bridge Rectifier

It is the most frequently-used circuit for electronic dc power supplies. It requires four diodes but the transformer used is not centre-tapped and has a maximum voltage of V_{sm} .

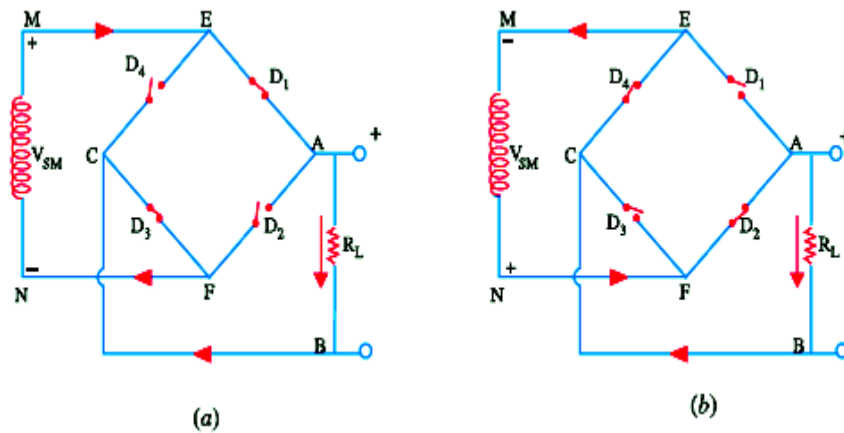(a) Working

During the positive input half-cycle, terminal M of the secondary is positive and N is negative as shown separately in Fig. below (a). Diodes D_1 and D_3 become forward-biased (ON) whereas D_2 and D_4 are reverse-biased (OFF). Hence, current flows along $MEABCFN$ producing a drop across RL .

During the negative input half-cycle, secondary terminal N becomes positive and M negative. Now, D_2 and D_4 are forward-biased. Circuit current flows along $NFABCEM$ as shown in Fig. below (b). The current keeps flowing through load resistance RL in the same direction AB during both half-cycles of the ac input supply. Consequently, point A of the bridge rectifier always acts as an anode and point C as cathode.



(b) Average and RMS Values

$$(i) \quad V_{dc} = 0.636 V_m \\ = 0.9V$$

$$(ii) \quad I_{dc} = \frac{2}{\pi} \frac{V_m}{R_L} \\ = 0.636 I_m \\ = 0.9 \times \frac{V}{R_L} = 0.9 I_{rms}$$

$$(iii) \quad I_{rms} = 0.707 I_m$$

$$(iv) \quad \text{form factor, } F = \frac{I_{rms}}{I_{av}} = \frac{I_{rms}}{I_{dc}} \\ = 1.11$$

(c) PIV:

In a full wave bridge rectifier, the PIV rating of each of the four diodes is V_m (not $2V_m$ as the case for ordinary full wave rectifier).

(d) Ripple factor (γ):

It is the same of for ordinary full wave rectifier

$$\gamma = 0.482$$

(e) Efficiency:

It is the same of for ordinary full wave rectifier

$\eta = 81.2\%$. *if diode resistance is neglected.*

(f) Advantages:

1. No centre-tap is required on the transformer.
2. Much smaller transformers are required.
3. It is suitable for high-voltage applications.
4. It has less *PIV* rating per diode.

The obvious disadvantage is the need for twice as many diodes as for the centre-tapped transformer version.

Diode Applications

Diode Clipper and Clamper Circuits

These are diode wave-shaping circuits *i.e.* circuits meant to control the shape of the voltage and current waveforms to suit various purposes. Each performs the wave-shaping function indicated by its name. The output of the clipping circuit appears as if a portion of the input signal were clipped off. But clamper circuits simply lams (*i.e.* lift up or down) the input signal to a different dc level.

Clippers

A clipping circuit requires a minimum of two components *i.e.* a diode and a resistor. Often, dc battery is also used to fix the clipping level. The input waveform can be clipped at different levels by simply changing the battery voltage and by