



# NORTON'S THEOREM

ninth lecture


Electrical engineering

Student name:

Department:

M.Sc. Ammar Altajer

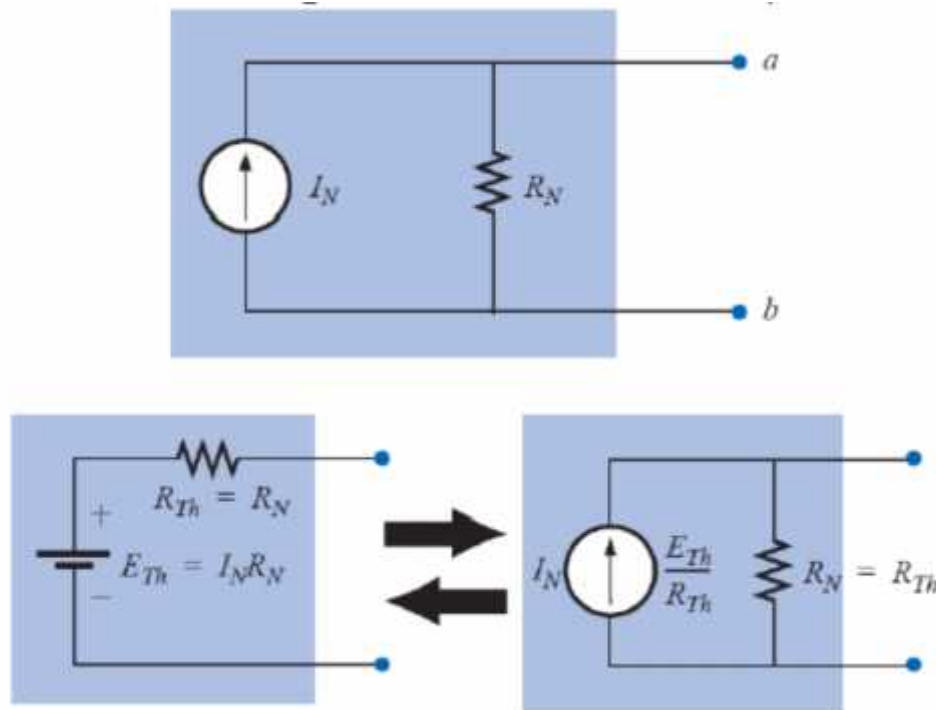
**Norton's Theorem** Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current source and a parallel resistor,




The steps leading to the proper values of  $I_N$  and  $R_N$  are now listed.

- Remove that portion of the network across which the Norton equivalent circuit is found.
- Mark the terminals of the remaining two-terminal network.
- Calculate  $R_N$  by first setting all sources to zero (voltage sources are replaced with short circuits and current sources with open circuits) and then finding the resultant resistance between the two marked terminals.
- Calculate  $I_N$  by first returning all sources to their original position and then finding the short-circuit current between the marked terminals.
- Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.

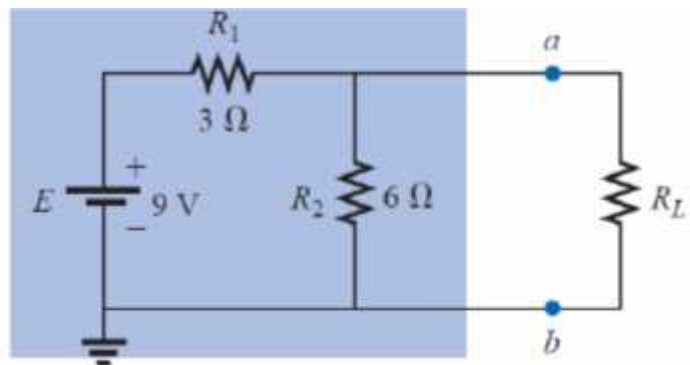
**Example 1:** Find the Norton equivalent circuit for the network.




*Solution:*

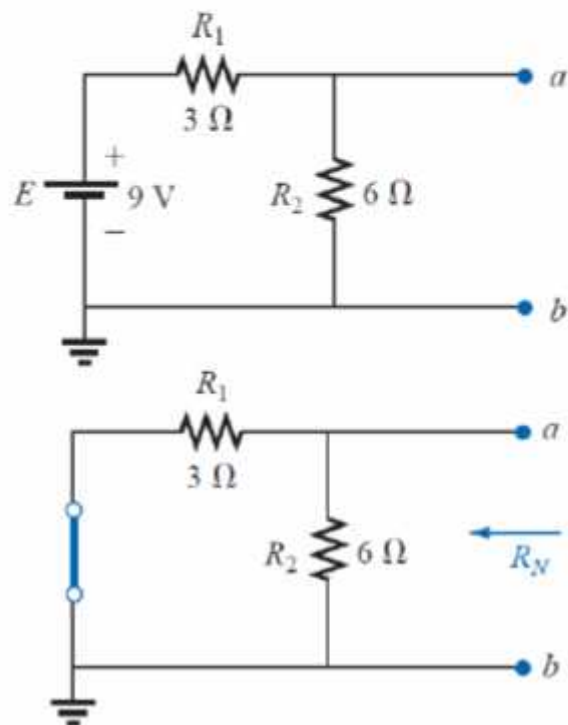

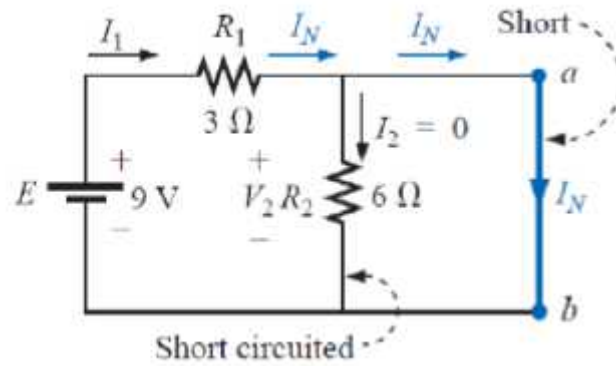
$$R_N = R_1 \parallel R_2 = 3 \, \Omega \parallel 6 \, \Omega = \frac{(3 \, \Omega)(6 \, \Omega)}{3 \, \Omega + 6 \, \Omega} = \frac{18 \, \Omega}{9} = 2 \, \Omega$$




$$V_2 = I_2 R_2 = (0)6\ \Omega = 0\ \text{V} \quad \Rightarrow \quad I_N = \frac{E}{R_1} = \frac{9\ \text{V}}{3\ \Omega} = 3\ \text{A}$$

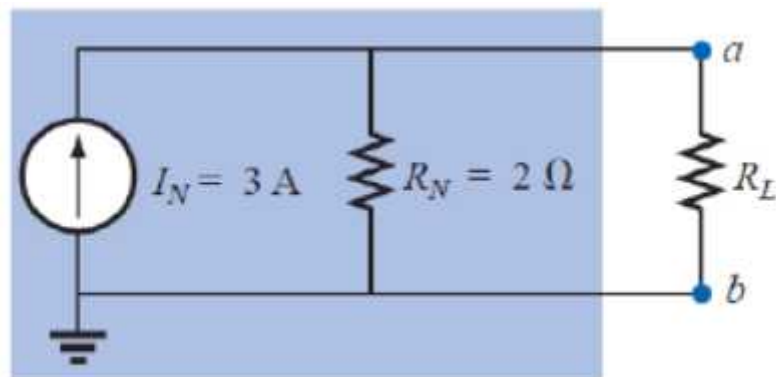

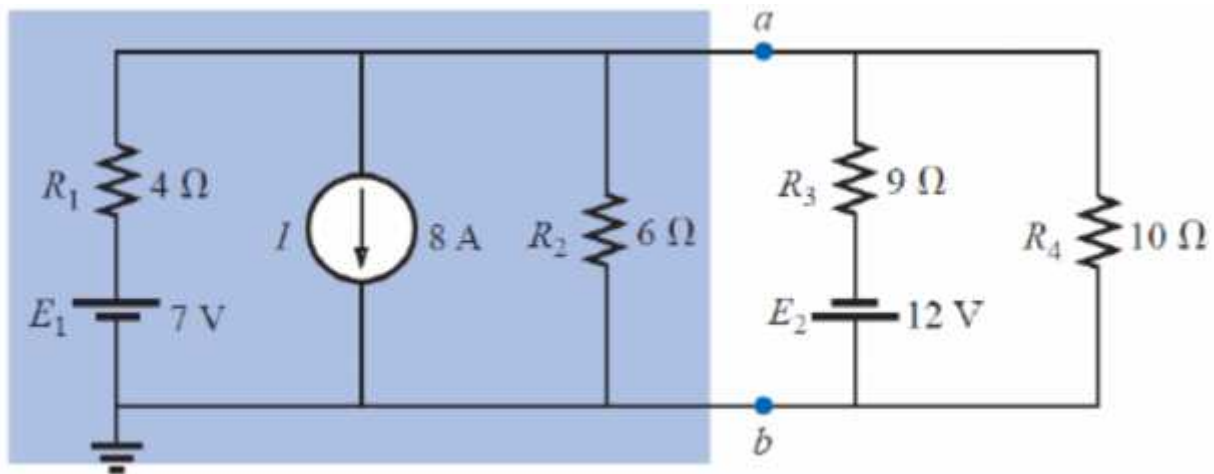
**Example 2 :** Find the Norton equivalent circuit for the portion of the network to the left of a-b.



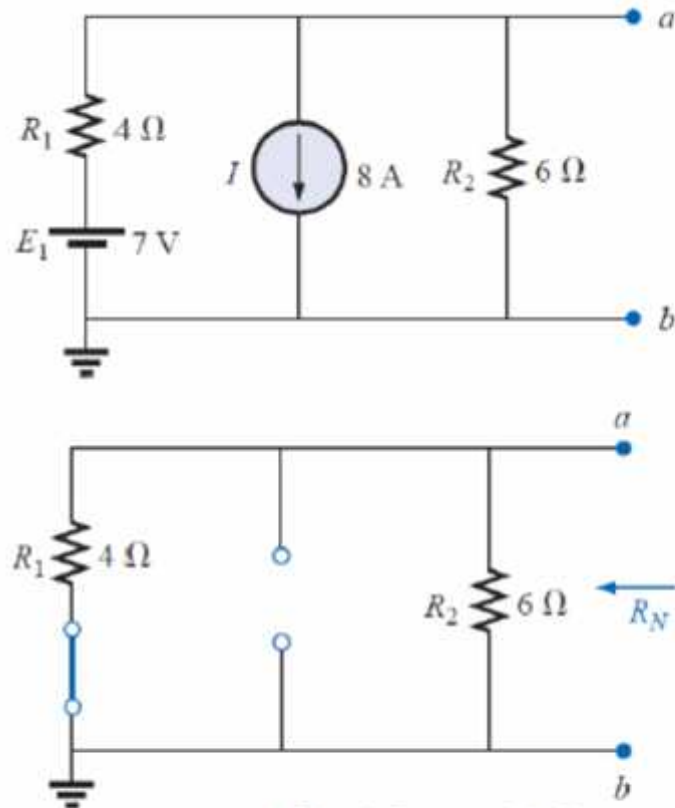


$$R_N = R_1 \parallel R_2 = 4 \, \Omega \parallel 6 \, \Omega = \frac{(4 \, \Omega)(6 \, \Omega)}{4 \, \Omega + 6 \, \Omega} = \frac{24 \, \Omega}{10} = 2.4 \, \Omega$$

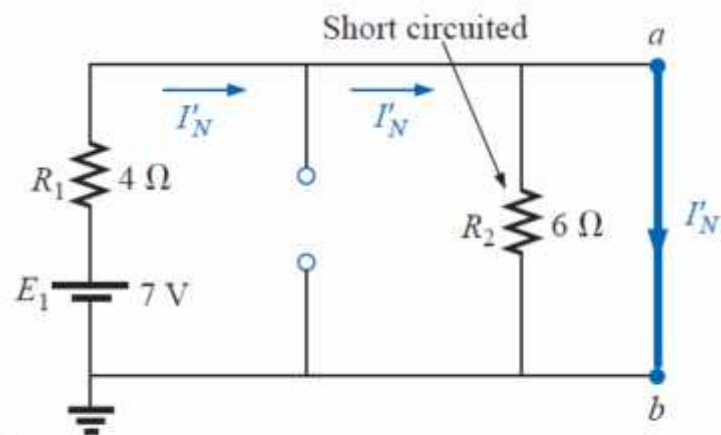1) (Using superposition) for the 7-V battery:



$$I'_N = \frac{E_1}{R_1} = \frac{7 \, \text{V}}{4 \, \Omega} = 1.75 \, \text{A}$$

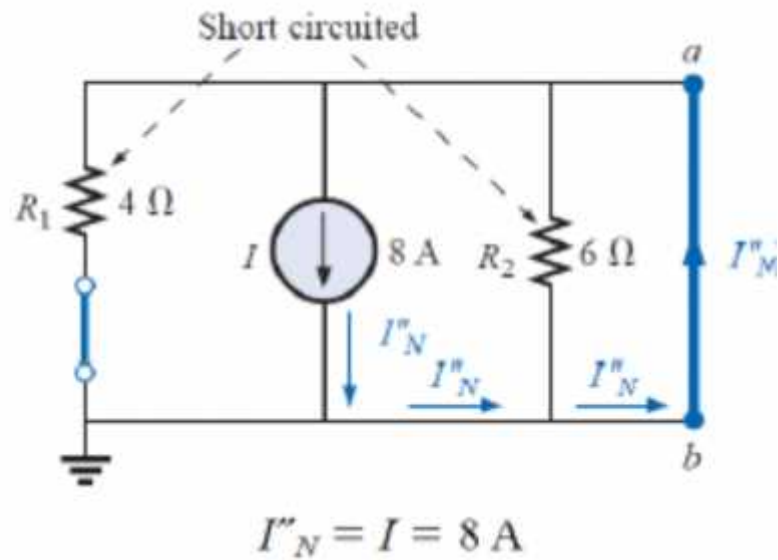2) (Using superposition) for the 8-A source



$$I_N = I''_N - I'_N = 8\text{ A} - 1.75\text{ A} = \mathbf{6.25\text{ A}}$$

